

Lecture 3

Rules:

$$1 + 1 = 1$$

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 \cdot 1 = 1$$

$$1 \cdot 0 = 0$$

$$0 \cdot 0 = 0$$

$$a + a = a$$

$$a \cdot 1 = a$$

$$a + 1 = 1$$

$$a \cdot a = a$$

$$a \cdot 0 = 0$$

$$a + 0 = a$$

$$ab + ac = a(b+c) \text{ (Distributive)}$$

$$ab + ab' = a(b+b') = a$$

$$ab' + a'b = a \oplus b$$

$$ab + a'b' = (a \oplus b)'$$

A	B	Q
0	0	0+0=0
0	1	0+1=1
1	0	1+0=1
1	1	0+0=0

} XOR.

$$a'b'c_i + ab'c_i + \underbrace{abc_i' + abc_i}$$

$$= a'b'c_i + ab'c_i + ab + abc_i$$

$$= a'b'c_i + ac_i + ab + abc_i$$

$$\begin{array}{l}
 a'b'c_i + ab'c_i + \underbrace{abc_i' + abc_i} \\
 + \underbrace{abc_i} + \underbrace{abc_i} \\
 \underbrace{bc_i} + ac_i + ab
 \end{array}$$

Simplification

Full Adder

When we add in decimal, we add in places

$$\begin{array}{r} 11 \\ 373 \\ + 198 \\ \hline 571 \end{array}$$

At any given place, we have two

inputs (e.g. 7 and 9) and possibly a carry.


$$\begin{array}{r} 11 \\ 373 \\ + 198 \\ \hline 571 \end{array}$$

\Rightarrow 3 inputs, call them a, b, c_i
(1st #, 2nd #, "carry in")

We get two outputs: the sum number

and a possible carry (s, c_o).
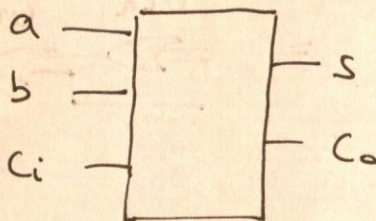
$$\begin{array}{r} 1 \\ 373 \\ + 198 \\ \hline 5(7)1 \end{array}$$



"Full adder" for only adding two bits and a carry.

e.g. $(a=1) + (b=0) + (c_i=1) \Rightarrow (s=0)$, with $(c_o=1)$.
"plus", not "OR"

$$\begin{array}{r} 1 \text{ carry} \\ 1 \\ + 0 \text{ a} \\ \quad b \\ \hline 10 \end{array}$$

Truth Table

a	b	c_i	s	c_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Equations

$$s = a'b'c_i + a'bc_i' + ab'c_i' + abc_i$$

$$= a'(b \oplus c_i) + a(b \oplus c_i)'$$


$$\boxed{s = a \oplus b \oplus c_i}$$

$$c_o = a'bc_i + ab'c_i + abc_i' + abc_i$$


+ $abc_i + abc_i$ (\leftarrow extras!)

$$\boxed{c_o = bc_i + ac_i + ab}$$

Not the only way to simplify!

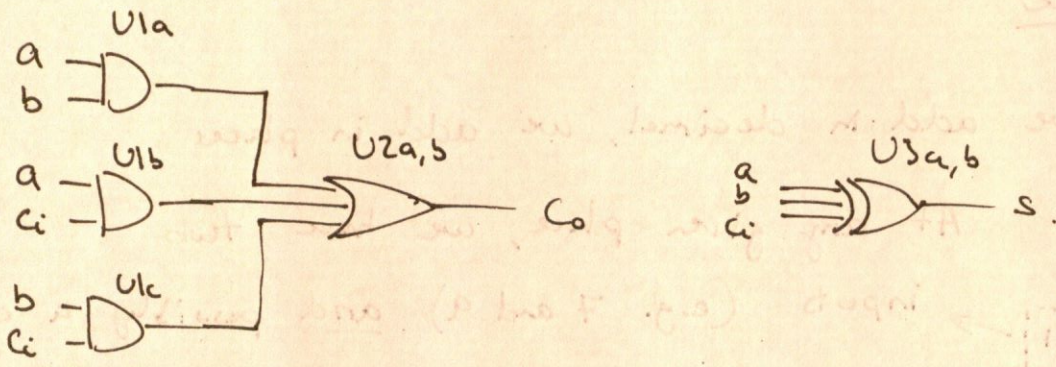

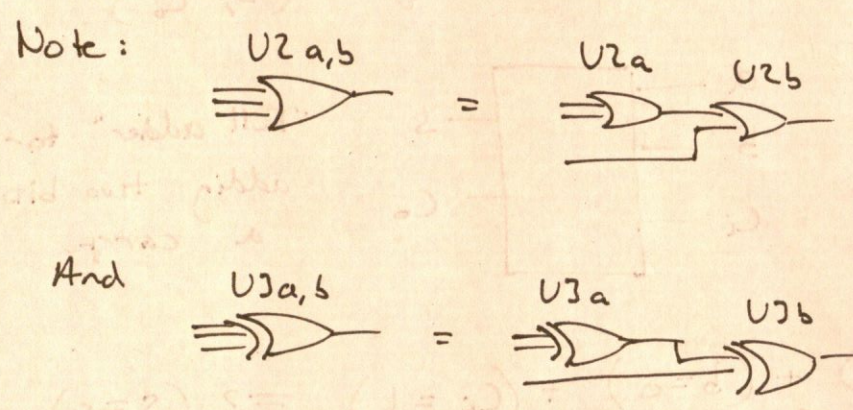- 74 HC 08 : Quad 2-input AND gate. (1) (use 3)
- 74 HC 32 : Quad 2-input OR gate. (1) (use 2)
- 74 HC 86 : Quad 2-input XOR gate. (1) (use 2)



$$s = a'b'ci + a'bc'i + ab'ci + abc'i$$

$$Co = a'(b'c) + a(bc)$$

$$s = abc + a'bc + ab'c + abc'$$

$$Co = a'b'c + a'bc + ab'c + abc$$

$$Co = a'b'c + a'bc + ab'c + abc$$

$$Co = abc + a'bc + ab'c + abc'$$

a	b	ci	s	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

not the end
way to simplify

Parity Bit Generator


"Even Parity"

b₂ b₁ b₀	P
0 0 0	0
0 0 1	1
0 1 0	1
0 1 1	0
1 0 0	1
1 0 1	0
1 1 0	0
1 1 1	1

$$P = b_2' b_1' b_0 + b_2' b_1 b_0' + b_2 b_1' b_0' + b_2 b_1 b_0$$

$$P = b_2' (b_1 \oplus b_0) + b_2 (b_1 \oplus b_0)'$$

$$P = b_2' \oplus b_1 \oplus b_0$$

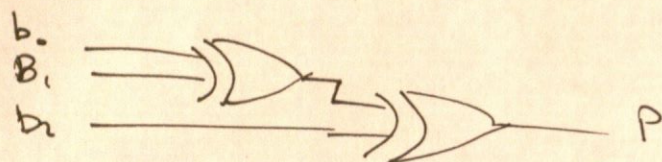

2.59


b_2	b_1	b_0	L
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$L = \underbrace{b_2' b_1' b_0' + b_2' b_1' b_0 + b_2' b_1 b_0'}_{}$$

$$L = b_2' b_1' b_0' + b_2' b_1' b_0 + b_2' b_1 b_0' + \boxed{b_2' b_1 b_0}$$

$$L = b_2' b_1' + b_2' b_0'$$

$$L = b_2' (b_1' + b_0')$$

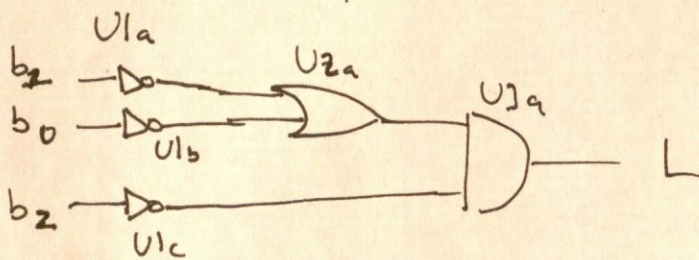

- 74 HC 04 Hex Inverter.
- 74 HC 08 Quad 2-input AND gate
- 74 HC 32 Quad 2-input OR gate.