 


# Lecture 4

So far we have only learned about combinational logic,




where the outputs are simple combinations based on inputs alone.

Combinational logic always responds the same way to inputs, regardless of past use (history). (e.g. light switch).


But suppose you want to do something sequentially, like cycle through a traffic light in a specified order. In this case, the response of the system depends both on inputs (e.g. pressing a button) and the current state (if the light is green, change to yellow; if yellow, change to red; if red, change to green).

The system must know its current state: it needs memory.

Consider the effect of feedback

 



(Bad) Example

 

But can't switch it back.



SR Latch

  


S "sets" the latch  
 R "resets" the latch.  
 Note that  $t = Q'$  during  
 Normal operation

 Problem with SR Latch  
 "Race Condition" commits the  
 Cardinal sin of digital electronics:  
 you don't know what the output  
 will be!




Can we prevent  $SR = "11"$  from occurring? - No.  
 Can we stop it from causing problems?




Enabled SR Latch  
 $C =$  Enable signal.

But: same problem if  $SR = "11"$ ,  
 which we still can't prevent.

### D-Latch

 


 "R" is now automatically  $S'$  - no problem!



While  $C$  is on, the latch is transparent: as  $S$  changes,  $Q$  will change. When  $C$  turns off,  $Q$  gets "locked in."

### Final Problem

 



While  $C$  is on, the  $IN$  signal will race through as many latches as it can until  $C$  turns off.

- 1) Not very elegant
- 2) Impossible to predict (!)




We need a solution that updates and locks in at the same time.

D Flip Flop "Edge Triggered"

  

↑  
update and  
lock in

 ↑  
Unaffected by changes in  
D, even when CLK is still on.



IN = 1, others start at 0

